

UNIVERSITY OF VICTORIA

CENG 241

DIGITAL DESIGN I

Lab 4 - 4-bit Binary Adder / Subtractor

Instructor:

Dr. Amirali BANIASADI

Teaching Assistant:

Grace HUI

Yves SENECHAL V00213837

Tyler STEPHEN V00812021

A01 - B03

June 22, 2015



University
of Victoria

1 Introduction

2 Discussion

2.1 Binary addition and subtraction using ones complement representation

A detailed discussion of how the 4-bit adder can be changed into 4-bit subtractor using XOR gates and only one control signal.

2.2 Building the hierarchical adder / subtractor

A general discussion of the design and the lab.

2.2.1 Half adder

 


Figure 1: Schematic of the half adder



 


Figure 2: Test results of the half adder

 

(a) Addition

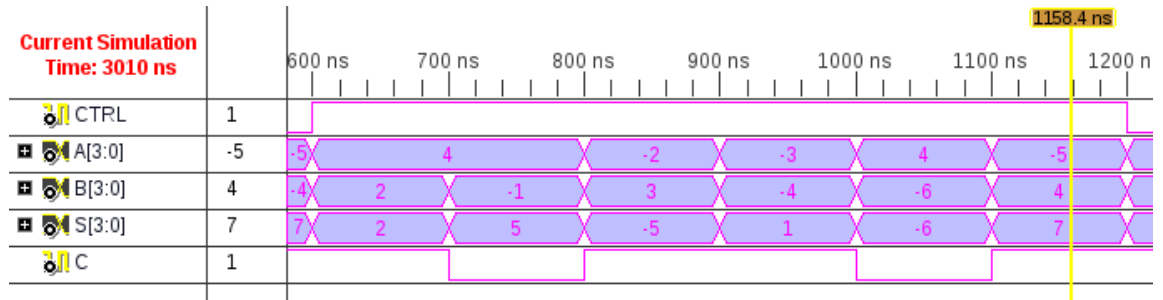

(b) Subtraction

Figure 6: Test results of the adder / subtractor

CTRL	A	B	S	C
0	1	4	5	0
0	-3	2	-1	0
0	-5	-1	-6	1
0	7	6	-3	0
0	-5	-5	7	1
1	4	2	2	1
1	4	-1	5	0
1	-2	3	-5	1
1	-3	-4	1	1
1	4	-6	-6	0
1	-5	4	7	1

Table 1: Output of the adder / subtractor for several test cases, in decimal

2.2.2 Full adder

2.2.3 Adder / subtractor

2.3 Verilog hierarchical adder / subtractor

2.3.1 Listings

```
module FA(A, B, CIN, S, COUT)
  input A, B, CIN;
  output S, COUT;

  HA U0(A, B, S0, C0);
  HA U1(S0, CIN, S, C1);

  assign COUT = C0 | C1;
```

FA.v


```
module AddSub(A0, A1, A2, A3, B0, B1, B2, B3, CTRL, S0, S1, S2, S3, C)
  input A0, A1, A2, A3, B0, B1, B2, B3, CTRL;
  output S0, S1, S2, S3, C;

  FA U0(A0, B0 ^ CTRL, CTRL, S0, COUT0);
  FA U1(A1, B1 ^ CTRL, COUT0, S1, COUT1);
  FA U2(A2, B2 ^ CTRL, COUT1, S2, COUT2);
  FA U3(A3, B3 ^ CTRL, COUT2, S3, C);
```


AddSub.v

2.3.2 Simulation results and delay times


3 Conclusion

 

(a) Functional simulation

 

(b) Post place timing

 

(c) Delay

Figure 7: Simulation results for the full adder written in verilog

 


Figure 8: Functional simulation results for adder / subtractor written in verilog