

UNIVERSITY OF VICTORIA

CENG 241

DIGITAL DESIGN I

Lab 2 - Using Xilinx ISE Tutorial

Instructor:

Dr. Amirali BANIASADI

Teaching Assistant:

Grace HUI

Yves SENECHAL V00213837

Tyler STEPHEN V00812021

A01 - B03

1 June, 2015



University
of Victoria

1 Introduction

2 Discussion

Figure 1: Complete schematic of a half adder

Figure 2: Functional simulation of a half adder

Figure 3: Verilog implementation of the half adder

```
module ha(X, Y, S, C);  
    input X;  
    input Y;  
    output S;  
    output C;  
    assign S = (X & (!Y)) | ((!X) & Y); // S = X XOR Y  
    assign C = X & Y; // C = X AND Y  
endmodule
```

Verilog implementation of a half adder

What are the digital design entry methods? Form your opinion, which one is the most efficient? Why?

What is the difference between a functional simulation and a timing simulation? Is a functional simulation sufficient enough to ensure the correctness of the design?

3 Conclusion