

UNIVERSITY OF VICTORIA

CENG 241

DIGITAL DESIGN I

---

## Lab 5 - Sequential Circuits: Flip-Flops and Counters

---

*Instructor:*

Dr. Amirali BANIASADI

*Teaching Assistant:*

Grace HUI

Yves SÉNÉCHAL V00213837

Tyler STEPHEN V00812021

A01 - B03

June 29, 2015



University  
of Victoria

## 1 Introduction

Sequential logic depends on present and past signals to determine the system's next state, hence sequential circuits have memory. The SR latches, D flip flops, T flip flops, and counters are examples of sequential circuits; they will be explored in this lab.

## 2 555 Timer

The required duty cycle of 50% and frequency of a few hertz were obtained from using resistors  $R_a = 330\Omega$ ,  $R_b = 1M\Omega$  and a capacitor  $C = 0.1\mu\Omega$ . From the following formulas,

$$\text{Clock frequency} = \frac{1.44}{(R_a + 2R_b)C}$$

$$\text{Duty cycle} = \frac{R_a + R_b}{R_a + 2R_b}$$

the expected clock frequency and duty cycle was 7.2Hz and 50% respectfully. Figure 1 shows the experimental frequency of 8.2Hz with a duty cycle of 54.08%. Resistance in the circuit leads and capacitance in the oscilloscope leads may account for these discrepancies.

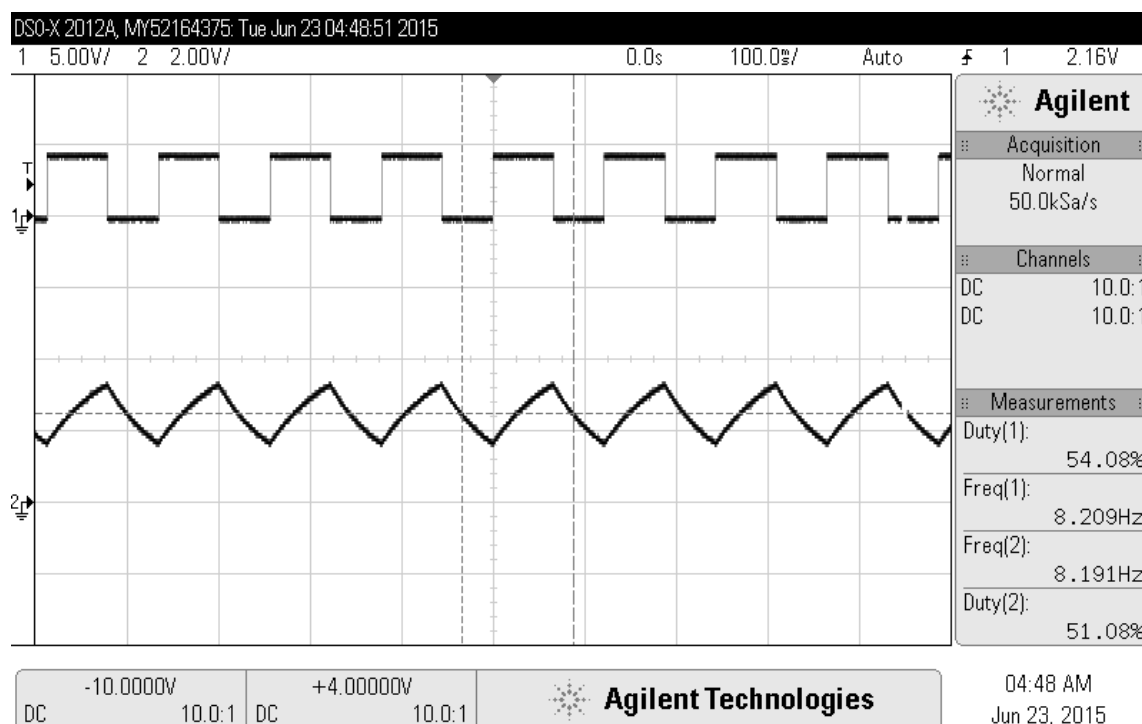


Figure 1: Output of the timer pin (top) and capacitor pin (bottom) for a 555 timer

## 3 RS Latch

- schematic of latch with two inverters on output
- screenshot of oscillations at 00/11
- how does frequency of oscillations relate to delay in circuit?

 


Figure 2: Oscillatory output of an RS latch in the indeterminate state

## 4 D Flip-Flop

- screenshot of D-FF changing on negative edge
- description of how D-FF works

## 5 T Flip-Flop

- screenshot for  $T=1$

## 6 Counter

- schematic of circuit as built in lab
- Explain why the output of the circuit is not in the range of 3 to 12 in the first few clock cycles.

## 7 Conclusion

 


Figure 3: The D flip-flop only updates its value on the falling edge

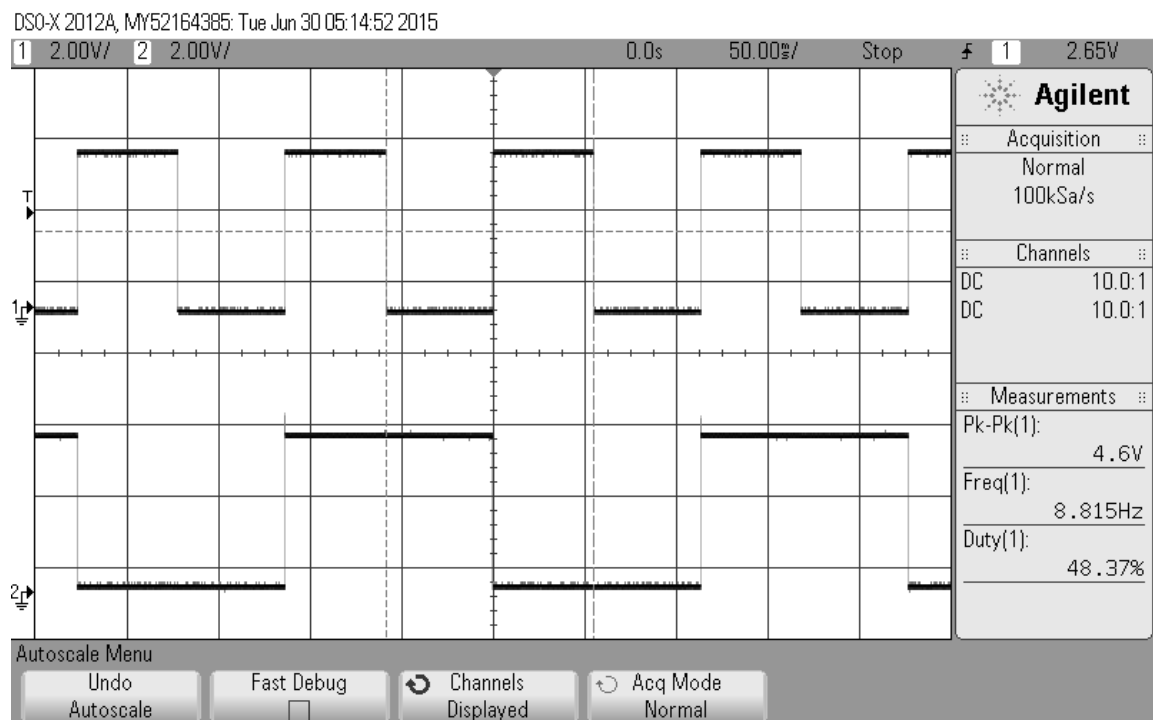


Figure 4: Output of a T flip-flop for  $T = 1$

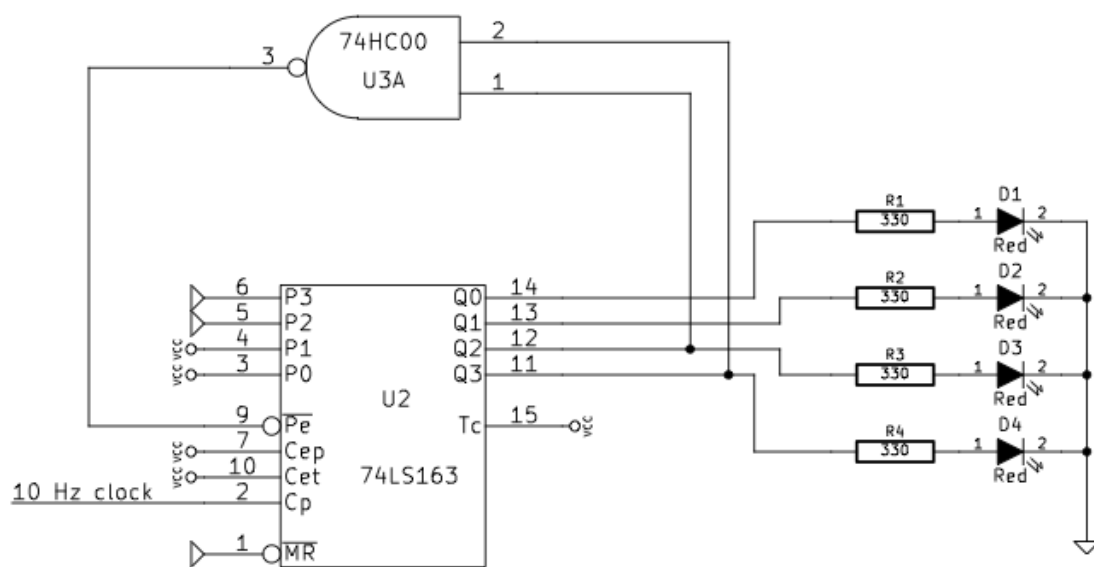


Figure 5: 74LS163 used to count 3 to 12 before resetting